

Section 3.5Electrical Circuits

Notation  $Q = Q(t)$  = instantaneous charge (Coulombs)

$I = I(t) = \frac{dQ}{dt}$  = current (Amps)

$R$  = resistance (Ohms)


$L$  = inductance (Henries)

$C$  = capacitance (Farads)

$E$  or  $V$  = EMF or Potential (Volts)


Laws

Ohms Law

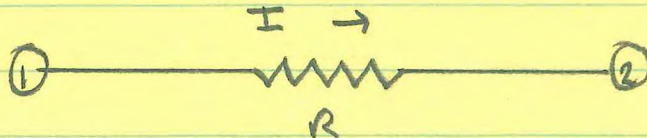


$$V_1 - V_2 = V_R = RI$$

Law of Inductance

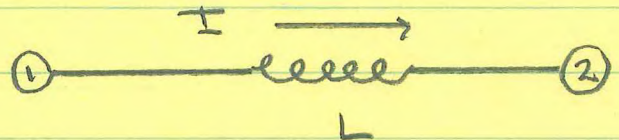

$$V_1 - V_2 = V_L = L \frac{dI}{dt}$$

Law of Capacitance

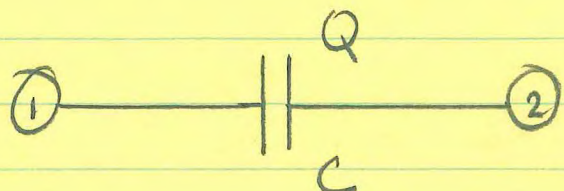


$$V_1 - V_2 = V_C = \frac{Q}{C}$$



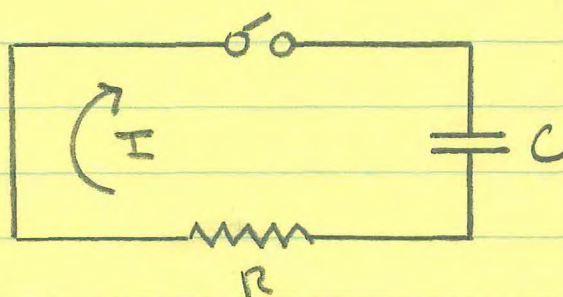Example!

At time  $t=0$  the key in the circuit opposite is closed. If the initial charge on the capacitor is  $Q_0$  Coulombs, describe the state of the circuit at time  $t>0$ .



Solution Let  $Q = Q(t)$  = charge on the capacitor at time  $t$ .

$$V_R + V_C = 0$$

$$RI + \frac{Q}{C} = 0$$

$$\therefore R \frac{dQ}{dt} + \frac{1}{C} Q = 0$$

$$\frac{dQ}{dt} + \frac{1}{RC} Q = 0 \quad \leftarrow \text{1st Order linear}$$

$$P(t) = e^{\int \frac{1}{RC} dt} = e^{t/RC}$$

Mult. above eqn by  $P$  :

$$e^{t/RC} \frac{dQ}{dt} + \frac{1}{RC} e^{t/RC} Q = 0$$

$$\frac{d}{dt} (e^{t/RC} Q) = 0$$

$$\underline{\text{Int}} \quad e^{t/RC} Q = A$$

$$Q = A e^{-t/RC}$$




$$t=0, Q=Q_0 : Q_0 = A e^0 \Rightarrow A = Q_0$$

$$\therefore Q = Q_0 e^{-t/RC}$$

$$\text{Further, } I = \frac{dQ}{dt} = -\frac{Q_0}{RC} e^{-t/RC}$$
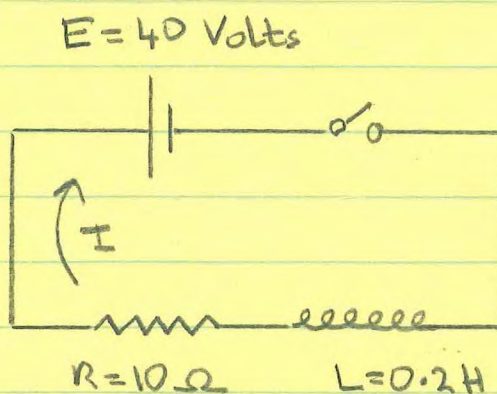
### Example 2

At time  $t=0$  the key in the circuit opposite is closed. If the initial current is zero, find the current at time  $t>0$ .



### Solution

$$V_R + V_L = E$$

$$RI + L \frac{dI}{dt} = E$$

$$10I + \frac{L}{5} \frac{dI}{dt} = 40$$

$$\frac{dI}{dt} + 50I = 200, \quad I(0) = 0$$

$$\mu(t) = e^{\int 50 dt} = e^{50t}$$

$$\text{Mult by } \mu : e^{50t} \frac{dI}{dt} + 50 e^{50t} I = 200 e^{50t}$$



$$\therefore \frac{d}{dt} [e^{50t} I] = 200 e^{50t}$$

$$\begin{aligned} \text{Int} \quad e^{50t} I &= \int 200 e^{50t} dt + A \\ &= 4 e^{50t} + A \end{aligned}$$

$$\therefore I = 4 + A e^{-50t}$$

$$\underline{t=0, I=0} \quad 0 = 4 + A(1) \Rightarrow A = -4$$

$$\therefore I = 4 - 4 e^{-50t}$$

Hw Page 121 #1's 1, 2