

Section 5.7Electrical Systems

Notation  $Q = Q(t)$  = instantaneous charge (Coulombs)

$$I = I(t) = \frac{dQ}{dt} = \text{current (Amps)}$$

$R$  = Resistance (Ohms)

$L$  = Inductance (Henries)

$C$  = Capacitance (Farads)

$E$  or  $V$  = Emf or Potential (Volts)

Ohms Law  $V_R = RI$

Law of Inductance  $V_L = L \frac{dI}{dt}$


Law of Capacitance  $V_C = \frac{Q}{C}$

Example 1

At time  $t=0$  the key in the circuit shown opposite is closed. If

the initial charge on the

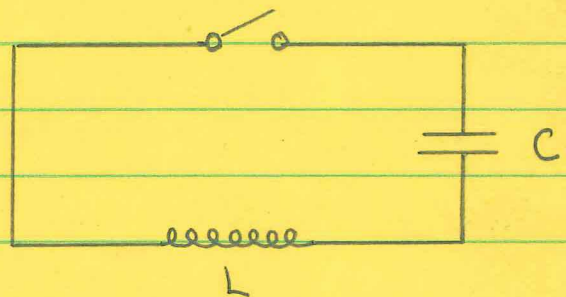capacitor is  $Q_0$  describe the state of the circuit at time  $t > 0$ .



Solution Let  $Q(t)$  be the charge on the capacitor at time  $t$ .

(2)

$$V_L + V_C = 0$$

$$L \frac{dI}{dt} + \frac{Q}{C} = 0$$

$$\therefore L \frac{d^2 Q}{dt^2} + \frac{Q}{C} = 0$$

$$\therefore \overset{\infty}{Q} + \omega^2 Q = 0, \quad \omega = \frac{1}{\sqrt{LC}}$$

Gen Soln  $Q(t) = A \cos \omega t + B \sin \omega t$

$t=0, Q=Q_0$   $Q_0 = A(1) + B(0) \Rightarrow A = Q_0$

$$\dot{Q}(t) = -A\omega \sin \omega t + B\omega \cos \omega t$$

$t=0, \dot{Q} = I = 0$   $0 = -A\omega(0) + B\omega(1) \Rightarrow B = 0$

$$\therefore Q(t) = Q_0 \cos \omega t = Q_0 \cos \left( \frac{t}{\sqrt{LC}} \right)$$

$$I(t) = \dot{Q}(t) = -\frac{Q_0}{\sqrt{LC}} \sin \left( \frac{t}{\sqrt{LC}} \right)$$

### Example 2

A circuit consists of an inductor of  $0.05 \text{ H}$ , a resistance of  $20 \Omega$ , a capacitor of  $100 \times 10^{-6} \text{ F}$ , and an emf of  $100 \text{ Volts}$ . Describe the state of the circuit at time  $t > 0$  if  $Q=0$  and  $I=0$  at  $t=0$ .



Solution

$$V_L + V_R + V_C = E$$

$$L \frac{dI}{dt} + RI + \frac{Q}{C} = E \quad \leftarrow \text{Replace } I \text{ by } \dot{Q}$$

$$L \ddot{Q} + R \dot{Q} + \frac{1}{C} Q = E$$

$$\frac{1}{20} \ddot{Q} + 20 \dot{Q} + \frac{1}{10^{-4}} Q = 100$$

$$\therefore \ddot{Q} + 400 \dot{Q} + 200,000 Q = 2,000$$

C.F.  $\ddot{Q} + 400 \dot{Q} + 200,000 Q = 0$

A.E.  $m^2 + 400m + 200,000 = 0$

$$\begin{aligned} m &= \frac{-400 \pm \sqrt{400^2 - 4(1)200,000}}{2(1)} \\ &= \frac{-400 \pm \sqrt{-640,000}}{2} \\ &= -200 \pm 400i \end{aligned}$$

$$Q_c(t) = A e^{-200t} \cos(400t) + B e^{-200t} \sin(400t)$$

P.I. Try  $Q_p = a$

$$\dot{Q}_p = 0$$

$$\ddot{Q}_p = 0$$

Substitute  $\ddot{Q}_p + 400 \dot{Q}_p + 200,000 Q_p = 2000$

$$0 + 0 + 200,000 a = 2,000$$

$$\therefore a = \frac{2,000}{200,000} = \frac{1}{100}$$

$$\therefore Q_p = \frac{1}{100}$$

Gen. Soln.  $Q(t) = e^{-200t} (A \cos 400t + B \sin 400t) + \frac{1}{100}$

$t=0, Q=0$   $0 = 1(A) + \frac{1}{100} \Rightarrow A = \frac{-1}{100}$

$$\dot{Q}(t) = e^{-200t} (-400A \sin 400t + 400B \cos 400t) - 200e^{-200t} (A \cos 400t + B \sin 400t)$$

$t=0, \dot{Q}=0$   $0 = 1(400B) - 200(A)$   
 $400B = 200A = -2$   
 $\therefore B = \frac{-1}{200}$

Part. Soln.  $Q(t) = \frac{-1}{200} e^{-200t} (2 \cos 400t + \sin 400t) + \frac{1}{100}$

$$I(t) = \dot{Q}(t) = e^{-200t} (-400A \sin 400t + 400B \cos 400t - 200A \cos 400t - 200B \sin 400t)$$

$$= e^{-200t} (4 \sin 400t - 2 \cos 400t + 2 \cos 200t + \sin 400t)$$

$$= 5 e^{-200t} \sin 400t$$

Example 3 Repeat Example 2 assuming that there is now a variable emf of  $E(t) = 100 \cos(200t)$ .



(5)

Solution  $\frac{1}{20} \ddot{Q} + 20 \dot{Q} + \frac{1}{10^{-4}} Q = 100 \cos(200t)$

$$\ddot{Q} + 400 \dot{Q} + 200,000 Q = 2,000 \cos(200t)$$

C.F.  $Q_c(t) = e^{-200t} (A \cos 400t + B \sin 400t)$

P.I. Try  $Q_p = a \cos(200t) + b \sin(200t)$

$$\dot{Q}_p = -200a \sin(200t) + 200b \cos(200t)$$

$$\ddot{Q}_p = -40,000a \cos(200t) - 40,000b \sin(200t)$$

Substitute  $\ddot{Q}_p + 400 \dot{Q}_p + 200,000 Q_p = 2,000 \cos(200t)$

$$(\cos 200t) [-40,000a + 80,000b + 200,000a] = 2000 \cos 200t$$

$$+ (\sin 200t) [-40,000b - 80,000a + 200,000b]$$

$$\left. \begin{array}{l} \cos 200t : 160,000a + 80,000b = 2000 \\ \sin 200t : -80,000a + 160,000b = 0 \end{array} \right\} \rightarrow a = 2b$$

$$160,000a + 40,000a = 2,000$$

$$a = \frac{2,000}{200,000} = \frac{1}{100}$$

$$b = \frac{1}{200}$$

$$\therefore Q_p(t) = \frac{1}{100} \cos(200t) + \frac{1}{200} \sin(200t)$$

Gen soln.  $Q = e^{-200t} (A \cos 400t + B \sin 400t)$

$$+ \frac{1}{100} \cos 200t + \frac{1}{200} \sin 200t$$

(6)

$$\underline{t=0, Q=0} \quad 0 = 1(A) + \frac{1}{100} \Rightarrow A = -\frac{1}{100}$$

$$\begin{aligned} \dot{Q}(t) = & e^{-200t} (-400A \sin 400t + 400B \cos 400t) \\ & - 200e^{-200t} (A \cos 400t + B \sin 400t) \\ & - 2 \sin 200t + \cos 200t \end{aligned}$$

$$\begin{aligned} \underline{t=0, \dot{Q}=0} \quad 0 &= 1(400B) - 200(A) + 1 \\ 0 &= 400B + 3 \\ B &= -\frac{3}{400} \end{aligned}$$

$$\begin{aligned} \underline{\text{Part Soln}} \quad Q = & -\frac{1}{400} e^{-200t} (4 \cos 400t + 3 \sin 400t) \\ & + \frac{1}{100} \cos 200t + \frac{1}{200} \sin 200t \end{aligned}$$

$$\begin{aligned} I(t) = \dot{Q}(t) = & e^{-200t} (4 \sin 400t - 3 \cos 400t) \\ & + e^{-200t} (2 \cos 400t + \frac{3}{2} \sin 400t) \\ & - 2 \sin 200t + \cos 200t \end{aligned}$$

$$\begin{aligned} = & e^{-200t} \left( \frac{11}{2} \sin 400t - \cos 400t \right) \\ & - 2 \sin 200t + \cos 200t \end{aligned}$$

HW. Pages 296-297, #'s 1, 3, 11, 13